

Digital Logic

or

Digital Circuit

or

Digital Electronics

Gate Notes

Standard : _____ Division : _____ Roll : _____

Subject: DIGITAL LOGIC



Rakesh Nama

Boolean Algebra + Logic gates

Boolean algebra is an algebraic structure defined on a set of elements together with two binary operators (\cdot) and ($+$).

→ A variable is a symbol - for example 'A' used to represent a logical quantity, whose value can be '0' or '1'.

→ The complement of a variable is the inverse of variable and is represented by an over bar, for example ' \bar{A} '.

→ A literal is a variable or the complement of variable.

- Closure: For any x and y in the alphabet A , $x+y$ and $x.y$ are also in A .

- Boolean value: The value of Boolean variable can be either '1' or '0'.

- Boolean Operators:

There are 4 Boolean operators -

(i) AND (\cdot) operator ($A \cdot B$)

(ii) OR ($+$) operator ($A+B$)

(iii) NOT (\bar{A}/A') operator

(iv) XOR (\oplus) operator ($A \oplus B = \bar{A}B + A\bar{B}$)

- Operator precedence:

The operator for evaluating Boolean expression is -

(i) parenthesis (ii) NOT (iii) AND (iv) OR

- Duality: If an expression contains only the operations AND, OR and NOT. Then the dual of that expression is by replacing each AND by OR, each OR by AND, all occurrences of '1' by '0' and all occurrences of '0' by 1. principle of duality is useful in determining the complement of a function.

logic expression: $(n \cdot y \cdot z) + (n \cdot y \cdot z') + (y \cdot z) + 0$

Duality of above logic expression is:

$$(n+y+z) \cdot (n+y+z') \cdot (y+z) \cdot 1.$$

- Boolean function:

→ Any Boolean functions can be from binary variables and the boolean operators \cdot , $+$ and ' (for AND, OR and NOT respectively).

→ for a given value of variable, the function can take only one value either '0' or '1'.

→ A Boolean function can be shown by a truth table. To show a function in a truth table we need a list of the 2^n combinations of 0's and 1's of the n binary variables and a column showing the combinations for which the function is equal to 1 or 0. So, the table will have 2^n rows and column for each input variable and the final output.

- A function can be specified or represented:-

- ① A truth table.
- ② A circuit.
- ③ A Boolean expression.
- ④ SOP (sum of products).
- ⑤ POS (product of sum).
- ⑥ Canonical SOP.
- ⑦ Canonical POS.

- Important Boolean operations over boolean values -

AND Operation

$$0 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

$$0 \cdot 1 = 1 \cdot 0 = 0$$

$$0' = 1$$

OR Operation

$$1 + 1 = 1$$

$$0 + 0 = 0$$

$$1 + 0 = 0 + 1 = 1$$

$$1' = 0$$

- Table of some basic theorems -

<u>law/theorem</u>	<u>law of addition</u>	<u>law of multiplication</u>
Identity law	$x + 0 = x$	$x \cdot 1 = x$
complement law	$x + \bar{x} = 1$	$x \cdot \bar{x} = 0$
Idempotent law	$x + x = x$	$x \cdot x = x$
Dominant law	$x + 1 = 1$	$x \cdot 0 = 0$
Involution law	$(x')' = x$	
Commutative law	$x + y = y + x$	$x \cdot y = y \cdot x$

Associative law

$$x + (y + z) = (x + y) + z$$

$$x \cdot (y \cdot z) = (x \cdot y) \cdot z$$

Distributive law

$$x + yz = (x + y)(x + z)$$

$$A(B+C) = AB + AC$$

DeMorgan's law

$$(x+y)' = x' \cdot y'$$

$$(x \cdot y)' = x' + y'$$

Absorption law

$$x + xy = x$$

$$x(x+y) = x$$

- Important theorem used in simplification

→ NOT - Operation theorem : $\bar{\bar{A}} = A$

→ AND - Operation theorem :

$$A \cdot A = A$$

$$A \cdot 1 = A$$

$$A \cdot 0 = 0$$

$$A \cdot \bar{A} = 0$$

→ OR - Operation theorem :

$$A + A = A$$

$$A + 1 = 1$$

$$A + 0 = A$$

$$A + \bar{A} = 1$$

- Distribution theorem

$$A + BC = (A+B)(A+C)$$

Note -

$$(A + \bar{A}B) \rightarrow (A+B)$$

$$(A + \bar{A}\bar{B}) \rightarrow (A+\bar{B})$$

$$(\bar{A} + A\bar{B}) \rightarrow (\bar{A}+B)$$

$$(\bar{A} + A\bar{B}) \rightarrow (\bar{A}+\bar{B})$$

- Demorgan's theorem:

$$\overline{(A+B+C)} = \bar{A} \cdot \bar{B} \cdot \bar{C}$$

$$\overline{(A \cdot B \cdot C)} = \bar{A} + \bar{B} + \bar{C}$$

- Transposition theorem:

$$(A+B)(A+C) = A+BC$$

• Consensus Theorem: This theorem is used to eliminate redundant term. It is applicable only when if a boolean function contain three variable. Each variable are used to times. only one variable is complemented or uncomplemented. Then the related terms so that complemented or uncomplemented variable is the answer -

Ex -

$$(I) AB + \bar{B}C + AC = AB + \bar{B}C.$$

$$(II) \bar{A}B + \bar{B}C + \bar{A}C = \bar{A}B + \bar{B}C.$$

$$(III) AB + \bar{A}C + BC = AB + \bar{A}C.$$

$$(IV) A\bar{B} + AC + BC = A\bar{B} + BC.$$

(i) + (ii) A(B + \bar{B}) = A

(iii) + (iv) A(\bar{B} + C) = A\bar{B} + AC

A + BC = A

* Problems on Boolean algebra =

* Simplify the following Boolean expressions to a minimum number of literals

LEVEL-1

$$(a) \bar{y}y + y\bar{y}$$

$$\Rightarrow \bar{y}(y+\bar{y})$$

$$\Rightarrow \bar{y} \cdot 1 \Rightarrow \bar{y}$$

$$(b) (\bar{x}+y)(\bar{x}+\bar{y})$$

$$\Rightarrow \bar{x}+\bar{y}\bar{y} \quad (\text{transposition theorem})$$

$$\Rightarrow \bar{x}+0 \Rightarrow \bar{x}$$

$$(c) \bar{y}z + \bar{y}\bar{z} + y\bar{z}$$

$$\Rightarrow \bar{y}(\bar{z}+\bar{z}) + \bar{y}z$$

$$\Rightarrow \bar{y} + \bar{y}z$$

$$\Rightarrow y(\bar{y}+\bar{z})$$

$$\Rightarrow y \cdot 1 \Rightarrow y$$

$$(d) (\bar{A}+B)(\bar{A}+\bar{B})$$

$$\Rightarrow (\bar{A}\bar{A}+B\bar{A}) (\bar{A}\bar{A}+B\bar{B}) (A\bar{B})$$

$$\Rightarrow 0 \cdot 0 = 0$$

LEVEL-2

$$(1) \bar{A}\bar{C} + ABC + \bar{A}\bar{C} + A\bar{B} \quad (\text{reduce to two literals})$$

$$\Rightarrow \bar{A}\bar{C}(\bar{A}+A) + A(\bar{B}+BC)$$

$$\Rightarrow \bar{C} + A(\bar{B}+BC)$$

$$\Rightarrow \bar{C} + A(\bar{B}+C)$$

$$\Rightarrow \bar{C} + A\bar{B} + AC$$

$$\Rightarrow (\bar{C}+A)(\bar{C}+C) + A\bar{B}$$

$$\Rightarrow (\bar{C}+A) + A\bar{B}$$

$$\Rightarrow A(1+B) + \bar{C}$$

$$\Rightarrow A + \bar{C}$$

(2) $\bar{A}B(\bar{D}+CD) + B(\bar{A}+\bar{A}CD) \rightarrow$ Reduce to one literals.

$$\rightarrow \bar{A}B(\bar{D}+C) + B(A+CD)$$

$$\Rightarrow B(\bar{A}\bar{D} + \bar{A}C + A + CD)$$

$$\Rightarrow B(\bar{A}\bar{D} + A + C + CD)$$

$$\Rightarrow B(A + \bar{D} + C + CD)$$

$$\Rightarrow B(A + C + \bar{D} + C) \quad [C + C = C]$$

$$\Rightarrow B(A + C + \bar{D})$$

$$\Rightarrow B(\bar{A} + \bar{C} + \bar{D}) \quad (\text{DeMorgan's law})$$

$$\Rightarrow B(\bar{A} \cdot \bar{C} \cdot \bar{D})$$

$$\bar{a} \cdot \bar{b} = \overline{(a+b)}$$

• Find the complement -

$$(a) F = \bar{u}\bar{y} + \bar{u}y$$

$$\rightarrow F_{\text{dual}} = (\bar{u} + \bar{y})(\bar{u} + y)$$

$$F_c = (\bar{u} + y)(x + \bar{y})$$

OR

$$\bar{F} = \overline{(\bar{u}\bar{y} + \bar{u}y)}$$

$$\Rightarrow \bar{\bar{u}}\bar{y} \cdot \bar{\bar{u}}y$$

$$\Rightarrow (\bar{u} + y)(x + \bar{y})$$

$$(b) F = (\bar{A}B + CD)\bar{E} + E$$

$$\rightarrow F_{\text{dual}} = \{(\bar{A} + B) \cdot (C + D) + \bar{E}\} \cdot E$$

$$E \cdot \bar{E} = 0$$

$$F_{\text{com}} = \{(\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D}) + E\} \bar{E}$$

$$= (\bar{A} + \bar{B})(\bar{C} + \bar{D})\bar{E}$$

$$\textcircled{c} \quad (\bar{n}+y+\bar{z}) \cdot (n+\bar{y}) \cdot (n+z)$$



$$f_3 = \bar{n} \cdot y \cdot \bar{z} + n \cdot \bar{y} + n \cdot z$$

$$F_{com} = \bar{n} \cdot \bar{y} \cdot z + \bar{n} \cdot y + \bar{n} \cdot \bar{z}$$

- List the truth table of the function

\textcircled{a}

$$F = ny + \bar{n}\bar{y} + \bar{y}z$$

$$= y(n+\bar{n}) + \bar{y}z$$

$$= y + \bar{y}z$$

$$F = y + z$$

table -

n	y	z	$F = y + z$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$\textcircled{b} \quad F = \bar{n}\bar{z} + yz$$



n	y	z	$f = \bar{n}\bar{z} + yz$
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Ans

$$\begin{aligned} 1 \cdot 1 + 0 \cdot 0 &= 1 \\ 1 \cdot 0 + 0 \cdot 1 &= 0 \end{aligned}$$

$$\begin{array}{l} 1 \\ 1 \\ 0 \\ + 1 \\ \hline 1 \end{array}$$

~~Ques.~~ (8) - Reduce the expression, $f = \overline{(A + \bar{B}C)} (A\bar{B} + ABC)$

$$\rightarrow f = \overline{(A + \bar{B}C)} (A\bar{B} + ABC)$$

$$\Rightarrow (\bar{A} \cdot \bar{B}C) (A(\bar{B} + BC))$$

$$\Rightarrow (\bar{A} (B + \bar{C})) (A(\bar{B} + C))$$

$$\Rightarrow (\bar{A}\bar{B} + \bar{A}\bar{C}) (A\bar{B} + AC)$$

$$\Rightarrow 0 + 0 + 0 + 0 \Rightarrow 0.$$

(9) Reduce the function to one literal.

$$F = (B + BC) (B + \bar{B}C) (B + D)$$

$$\rightarrow f = (B + BC) (B + \bar{B}C) (B + D)$$

$$\Rightarrow B(1+C) ((B + \bar{B})(B + C)) (B + D)$$

$$\Rightarrow B(1+C) (B + C) (B + D)$$

$$\Rightarrow B(B + C) (B + D)$$

$$\Rightarrow B(B + BD + BC + CD)$$

$$\Rightarrow B(B + CD)$$

$$\Rightarrow B + BCD$$

$$\Rightarrow B(1 + CD)$$

$$\Rightarrow B.$$

(10) Reduce the Boolean expression -

$$F = AB + A(B+C) + \bar{B}(B+D)$$

$$\Rightarrow AB + AB + AC + \cancel{\bar{B}B} + \bar{B}D$$

~~AB~~

$$\Rightarrow AB + AC + \bar{B}D$$

Q) Reduce the boolean expression -

$$F = \overline{A}B + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}\overline{C}\overline{D}\overline{E}$$

$$\Rightarrow \overline{A}B(1 + \overline{C} + C\overline{D} + \overline{C}\overline{D}\overline{E})$$

$$\Rightarrow \overline{A}B \cdot 1$$

$$\Rightarrow \overline{A}B.$$

Q) Reduce the boolean expression -

$$F = AB + \overline{A}C + A\overline{B}C(AB + C)$$

$$\Rightarrow AB + \overline{A} + \overline{C} + 0 + A\overline{B}C$$

$$\Rightarrow \overline{A} + B + \overline{C} + A\overline{B}C$$

$$\Rightarrow \overline{A} + B + \overline{C} + A\overline{B}$$

$$\Rightarrow \overline{A} + B + \overline{C} + A$$

$$\Rightarrow 1 + B + \overline{C}$$

$$\Rightarrow 1.$$

Q) Reduce the given boolean ex -

$$F = \overline{\overline{A}\overline{B}} + \overline{A} + A\overline{B}$$

$$\Rightarrow (\overline{A}B) \cdot (\overline{A} + A\overline{B})$$

$$\Rightarrow (AB) \cdot (\overline{A} + B)$$

$$\Rightarrow (AB) \cdot (A\overline{B})$$

$$= 0.$$

$$A + B C = (A+B)(A+C)$$

$$\overline{A} + B = A \cdot \overline{B}$$

$$0 \cdot 0 = 0$$

$$0 + 0 = 0$$

⑥ If $x=1$ in the logic function -

$$\left[x + z \{ \bar{y} + (\bar{z} + x\bar{y}) \} \right] \{ \bar{x} + \bar{z} (x+y) \} = 1$$

$$(a) y=2 \quad (b) y=\bar{z} \quad (c) z=1 \quad (d) z=0.$$

$$\rightarrow \left[1 + z \{ \bar{y} + (\bar{z} + x\bar{y}) \} \right] \{ 0 + \bar{z} (1+y) \} = 1$$

$$\Rightarrow 1 \cdot \bar{z} = 1$$

$$\Rightarrow \bar{z} = 1$$

$$z = 0$$

⑦ The boolean expression -

$$Y = \bar{A}\bar{B}\bar{C}D + \bar{A}BC\bar{D} + A\bar{B}\bar{C}D + AB\bar{C}\bar{D}$$

reduce to

$$(a) Y = \bar{A}\bar{B}\bar{C}D \quad \bar{A}B\bar{C} \quad A\bar{C}D$$

$$(b) Y = \bar{A}\bar{B}\bar{C}D \quad B\bar{C} \quad A\bar{B}CD$$

$$(c) Y = \bar{A}\bar{B}\bar{C}D \quad \bar{B}\bar{C}D \quad A\bar{B}CD$$

$$(d) \checkmark Y = \bar{A}\bar{B}\bar{C}D \quad \bar{B}\bar{C}D \quad A\bar{B}CD$$

$$\rightarrow \text{So } Y = \underline{\bar{A}\bar{B}\bar{C}D} + \underline{\bar{A}BC\bar{D}} + \underline{A\bar{B}\bar{C}D} + \underline{AB\bar{C}\bar{D}}$$

$$= \bar{B}\bar{C}D (A + \bar{A}) + \bar{A}BC\bar{D} + A\bar{B}\bar{C}\bar{D}$$

$$= \bar{B}\bar{C}D + \bar{A}BC\bar{D} + A\bar{B}\bar{C}\bar{D}$$

$$⑧ W = R + \bar{P}Q + \bar{R}S.$$

$$X = P\bar{Q} \bar{R} \bar{S} + \bar{P} \bar{Q} \bar{R} S + P \bar{Q} R \bar{S}$$

$$Y = \bar{R}S + PR + \bar{P} \bar{Q} + \bar{P} Q$$

$$Z = R + S + P\bar{Q} + \bar{P} \bar{Q} \bar{R} + P \bar{Q} S$$

then

$$(a) W = Z, X = \bar{Z} \quad (b) W = Z, X = Y$$

$$(c) W = Y, X = \bar{Z} \quad (d) W = Y = \bar{Z}$$

$$W = \underline{R + \bar{P}S + \bar{R}S}$$

$$= (R + \bar{R})(R + S) + \bar{P}S$$

$$A + B C = (A + B)(A + C)$$

$$= R + S + \bar{P}S \quad \text{--- (I)}$$

$$X = P \bar{S} \bar{R} \bar{S} + \bar{P} \bar{S} \bar{R} \bar{S} + P \bar{S} \bar{R} \bar{S}$$

$$= P \bar{S} \bar{R} \bar{S} + \bar{S} \bar{R} \bar{S} (\bar{P} + P)$$

$$= \bar{R} \bar{S} (P \bar{S} + \bar{S})$$

$$= \bar{R} \bar{S} (P + \bar{S})$$

$$= \bar{R} \bar{S} P + \bar{R} \bar{S} \bar{S} \quad \text{--- (II)}$$

$$Y = RS + \underline{PR + \bar{P}S + \bar{P}S}$$

$$= RS + \underline{PR + \bar{P}S}$$

$$= RS + \bar{P}R \bar{P}S$$

$$= RS + (\bar{P} + \bar{R})(P + \bar{S})$$

$$= \cancel{RS} + \bar{P}S + \bar{P}R + \bar{R}S \quad \text{--- (III)}$$

$$Z = R + S + \underline{P \bar{S} + \bar{P} \bar{S} \bar{R} + \bar{P} \bar{S} \bar{R}}$$

$$= R + S + \underline{P(S + \bar{S}\bar{R}) + \bar{P} \bar{S} \bar{R}}$$

$$= R + S + \underline{P(S + \bar{S}) + \bar{P} \bar{S} \bar{R}}$$

$$= R + S + \underline{\bar{P}S + \bar{P}\bar{S} + \bar{P} \bar{S} \bar{R}}$$

$$= R + S + \underline{\bar{P}S \cdot \bar{P}\bar{S} \cdot \bar{P} \bar{S} \bar{R}}$$

$$= R + S + (\bar{P} + \bar{S})(\bar{P} + S)(P + B + R)$$

$$\cancel{EOR + L(P + S)(P + R \bar{P}C + SP + S \bar{Q} + HS)}$$

$$\cancel{EOR + L(P + S)(P + R \bar{P}C + SP + S \bar{Q} + HS)}$$

$$= R + S + (\bar{P} + \bar{P}S + \bar{Q}\bar{P} + \bar{B}S)(P + B + R)$$

$$= R + S + (\bar{P} + \bar{B}\bar{P} + \bar{B}S)(P + B + R)$$

$$= R + S + \overline{P}B + \overline{P}R + \overline{B}\overline{P}R + P\overline{B}S + \overline{B}SR$$

$$= \cancel{R} + \cancel{S} + \overline{P}B + \cancel{\overline{P}R} + P\overline{B}S + \overline{B}RS$$

~~for rates~~

$$= R + \cancel{S} + R + \overline{P}R + \overline{B}RS + \cancel{P\overline{B}S} + P\overline{B}S + \overline{P}B$$

$$= R[1 + \overline{P} + \overline{B}S] + S[1 + P\overline{B}] + \overline{P}B.$$

$$Z = R + S + \overline{P}B. \quad \boxed{W}$$

here, eqn ① and ④ same equation.

$$\boxed{W = Z},$$

$$Z_{\text{dual}} = RS(\overline{P}B)$$

$$X = \overline{RS}(P + \overline{B}).$$

$$Z = R + S + \overline{P}B.$$

$$Z_C = \overline{RS}(P + \overline{B})$$

$$\overline{Z}_{\text{dual}} = \overline{R + S + \overline{P}B}$$

$$= \overline{RS}(P + \overline{B})$$

$$\boxed{X = \overline{Z}}$$

atlantis

Date _____

Page _____

1A

- Logic gates = A logic gate is an idealised or physical device implementing a Boolean function, that is, it performs a logical operation in one or more logic I/P and produce a single logic O/P.

Logic gates can be classified as -

- (I) NOT, AND, OR are basic gates.
- (II) NAND, NOR are universal gates.
- (III) EXOR, EXNOR are arithmetic circuit or code converters or comparators.

- Not gate (Inverter) :

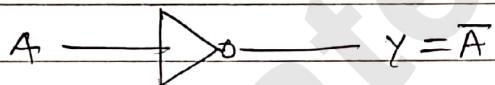


table -

I/P	O/P
A	$Y = \bar{A}$
0	1
1	0

- AND gate -

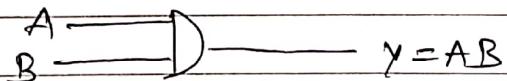


table -

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


Properties of AND gate -

→ follow Commutative and
Associative law.

$$AB = BA$$

$$ABC = A(BC) = (AC)B,$$

• OR Gate -

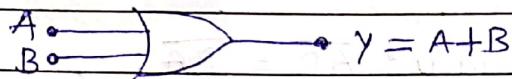

(OR gate symbol)

Truth table of OR Gate :


Inputs		Output
A	B	$y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Properties of OR logic -

(i) Commutative law $= (A + B) = (B + A)$.

(ii) Associative law $= (A + B + C) = (A + B) + C = B + (A + C)$.

• NAND Gate :

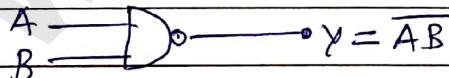

(NAND gate symbol)

Truth table of NAND gate -


Input		Output
A	B	$y = \overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

properties of NAND gate -

(1) Commutative law : $\overline{AB} = \overline{BA}$.

(2) Associative law : $\overline{ABC} \neq \overline{\overline{AB}C}$.

• NOR gate -

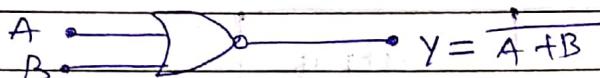


(NOR gate symbol)

Truth table of NOR gate -

Input		Output
A	B	$y = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

→ NOR gate follows commutative law but not follows associative law.

• Ex-OR Gate :

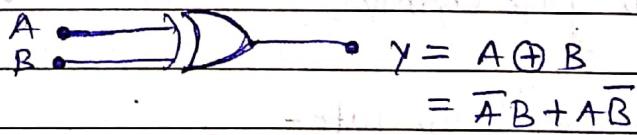

$$y = A \oplus B$$

$$= \overline{AB} + A\overline{B}$$

(Ex-OR gate symbol)

Truth table of Ex-OR Gate -

Input		Output
A	B	$y = A \oplus B = \overline{AB} + A\overline{B}$
0	0	0
0	1	1
1	0	1
1	1	0

Properties of EX-OR Gate -

- Enable Input = 0
- Disable Input = 1
- It is called staircase switch.
- When both input are different, then output become high or logic '1'.
- When both input are same, then output become low or logic '0'.
- Arithmetic gate. • Inequality detector.

Note: $A \oplus A = 0$


$$A \oplus \overline{A} = 1$$

$$A \oplus 0 = A$$

$$A \oplus 1 = \overline{A}$$

→ follow Associative and Commutative both law.

• Ex-NOR Gate:

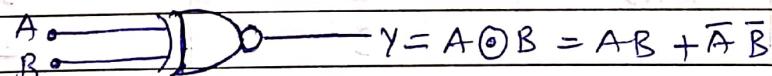

$y = A \odot B = AB + \overline{A}\overline{B}$
(Ex-NOR gate symbol)

Truth table of Ex-NOR Gate -

Input		Output
A	B	$y = A \oplus B = AB + \bar{A}\bar{B}$
0	0	1
0	1	0
1	0	0
1	1	1

properties of EXNOR Gate -

- Enable Input = 1
- Disable Input = 0
- When both the input are same, then output become high or logic '1'.
- When both the input are diff, then output become low or logic '0'.
- Equality detector.
- NAND and NOR Gate universal gate -

Logic Gate	Required no. of NAND Gate	Required no. of NOR Gate
NOT	1	1
AND	2	3
OR	3	2
EXOR	4	5
EXNOR	5	4

• Implementation of NAND Gate =

procedure to implement Boolean functions —

→ Step-1: Take complement of given function & apply DeMorgan's theorem.

→ Step-2: Take one more time complement to get original function.
And implement using NAND gates.

• NAND Gate as universal gate —

(i) NOT gate:

$$Y = \overline{A}$$

$$\text{NAND } \otimes, Y = \overline{A \cdot B} = \overline{A} \cdot \overline{A} = \overline{A}$$



(ii) AND gate:

$$Y = A \cdot B$$

$$\text{NAND } \otimes, Y = \overline{A \cdot B}$$




(iii) OR gate:

$$Y = A + B$$


$$\text{Step-1}, \overline{Y} = \overline{A+B} = \overline{A} \cdot \overline{B}$$
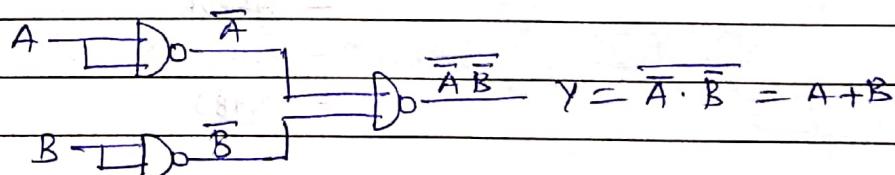
$$\text{Step-2}, \overline{\overline{Y}} = \overline{\overline{A} \cdot \overline{B}}$$



(iv) NOR gate:

$$Y = \overline{A+B}$$

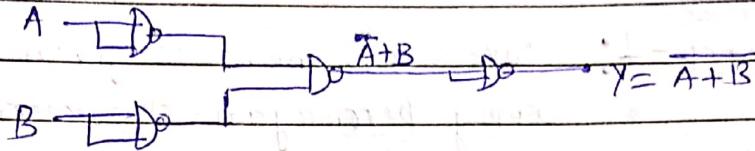(v) Ex-OR gate:

$$Y = A \oplus B = \overline{AB} + A\overline{B}$$

$$\text{S-1: } \overline{Y} = \overline{\overline{AB}} + A\overline{B}$$

$$= \overline{AB} \cdot \overline{A\overline{B}}$$

$$\text{S-2: } \overline{Y} = \overline{\overline{AB} \cdot A\overline{B}}$$

$$\begin{aligned}
 & A \xrightarrow{\text{D}} \overline{AB} \\
 & B \xrightarrow{\text{D}} \overline{AB} \\
 & A \xrightarrow{\text{D}} \overline{AB} \\
 & B \xrightarrow{\text{D}} \overline{AB}
 \end{aligned}
 \quad
 \begin{aligned}
 & \overline{AB} \xrightarrow{\text{D}} A \\
 & \overline{AB} \cdot A \xrightarrow{\text{D}} \overline{AB} \cdot \overline{AB} \\
 & = (A+\overline{B}) \cdot (\overline{A}+B) \quad \checkmark \\
 & = (A+\overline{B}) + (\overline{A}+B) \\
 & = \overline{AB} + A\overline{B}.
 \end{aligned}$$

$$\begin{aligned}
 & A \xrightarrow{\text{D}} \overline{AB} \cdot A = (\overline{A}+B) \\
 & B \xrightarrow{\text{D}} \overline{AB} \\
 & \overline{AB} \xrightarrow{\text{D}} \overline{AB} \cdot B \\
 & = \overline{(\overline{A}+B)} \cdot B \\
 & = \overline{\overline{AB}} \\
 & = (A+\overline{B})
 \end{aligned}$$

(VI) Ex-NOR gate:




$$y = A \odot B$$

$$= AB + \bar{A}\bar{B}$$

$$\text{Step-1: } \bar{y} = \overline{AB + \bar{A}\bar{B}}$$

$$\bar{y} = \overline{AB} \cdot \overline{\bar{A}\bar{B}}$$
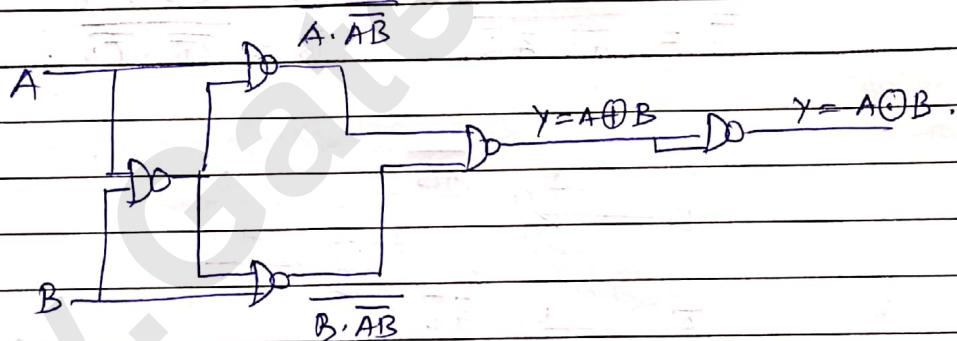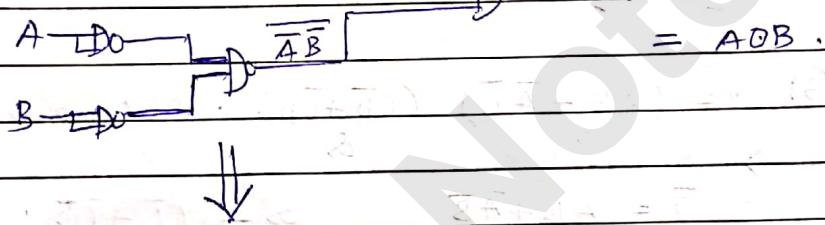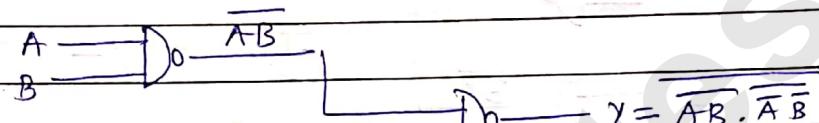
$$\text{Step-2: } \bar{y} = \overline{\overline{AB} \cdot \overline{\bar{A}\bar{B}}}$$



5 NAND gate required to implement one Ex-NOR gate.


Implementation of Boolean functions using only NAND gates -

$$(i) y = AB + CD$$

$$\text{Step-1: } \bar{y} = \overline{AB + CD}$$

$$= \overline{AB} \cdot \overline{CD}$$
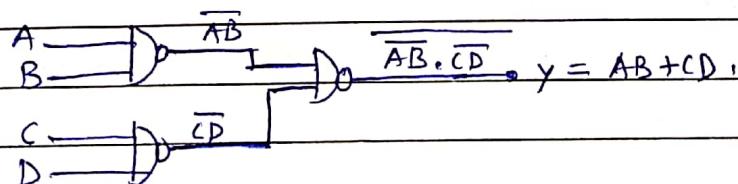
$$\text{Step-2: } \bar{y} = \overline{\overline{AB} \cdot \overline{CD}}$$



To Get Full Content

Click of the below link given
in this page



www.GateNotes.in

or

visit:www.gatenotes.in